

Tutorial-1

1. State Kirchhoff's law. Find the current in $3\ \Omega$ resistance in fig.1 by loop current method and verify the answer by node voltage method.

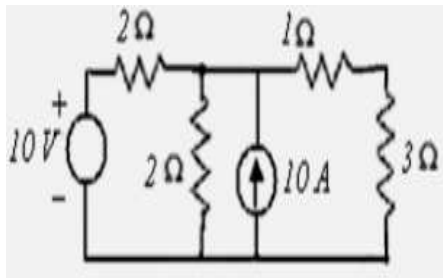


Fig. 1

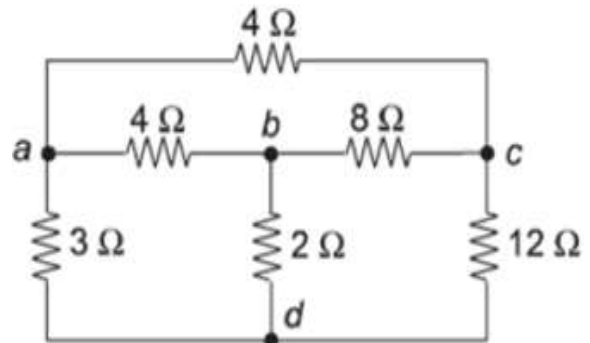


Fig. 2

2. Reduce the network of fig. 2 to obtain the equivalent resistance as seen between nodes a and d.
3. Find current I in the circuit shown in fig. 3. All resistances are in ohms.

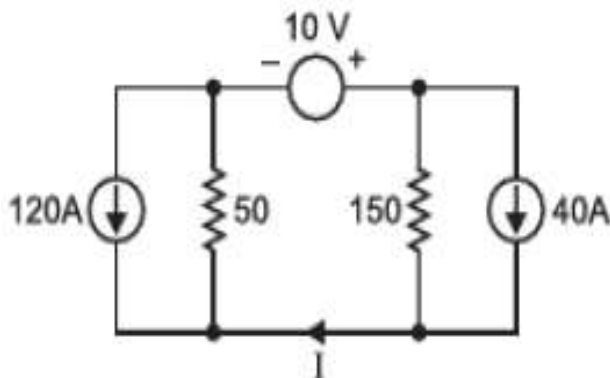


Fig. 3

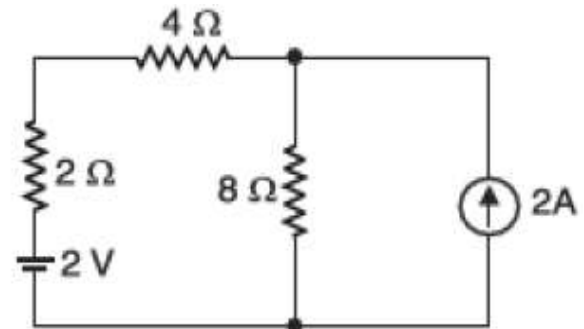


Fig. 4

4. Use nodal analysis to find the voltage across and current through $4\ \Omega$ resistor in fig. 4.
5. Find the current and voltage across $2\ \Omega$ resistance in the following fig. 5.

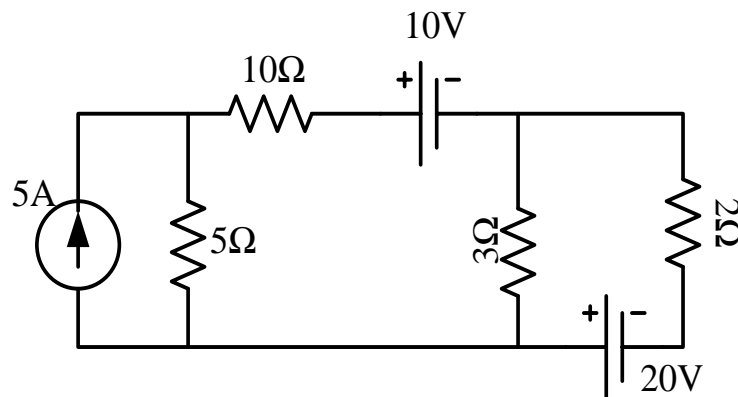


Fig. 5

(Ans: 5A, 10V)

6. Use nodal analysis to find the currents in $3\ \Omega$ and $4\ \Omega$ resistors of the circuit shown in fig. 6.

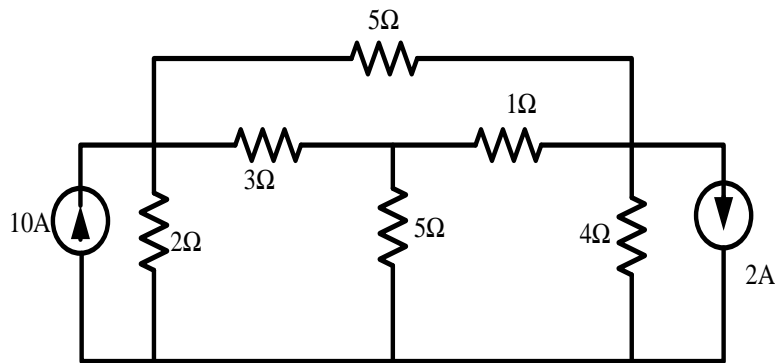


Fig. 6

(Ans: $I_2 = 2.3A$ $I_4 = 1.29A$)

7. Using delta to Star Transformation determines the resistance between terminals a-b and the total power drawn from the supply in the circuit shown in fig.7.

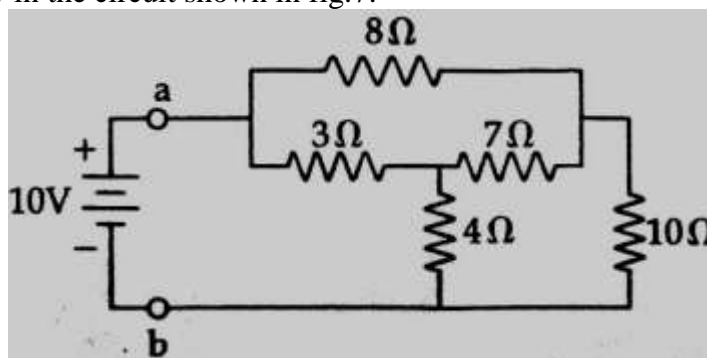


Fig. 7

(Ans: $R_{eq} = 5.031 \Omega$, $P = 19.873 W$)

8. Find I_1 , I_2 and I_3 in the network shown in fig. 8 below using loop current method.

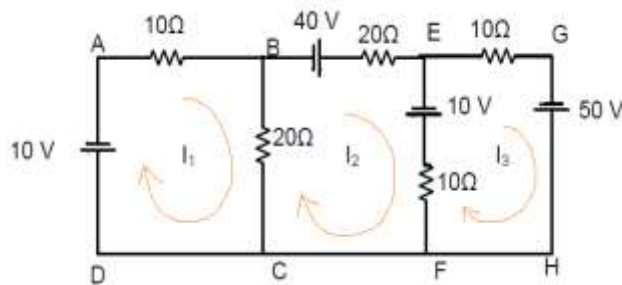


Fig. 8

(Ans: $I_1 = 1A$, $I_2 = 2A$, $I_3 = 3A$)

9. Use nodal analysis to find currents in the different branches of the circuit shown in fig. 9.

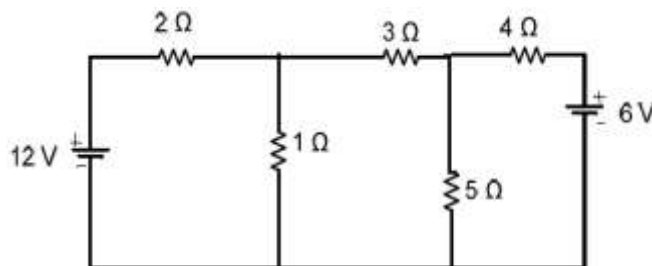


Fig. 9

(Ans: $I_{R2} = 4.038A$, $I_{R1} = 3.924A$, $I_{R3} = 0.1133A$, $I_{R5} = 0.7168A$, $I_{R4} = 0.604A$)

10. For the circuit shown in fig. 10,

- i. Calculate V_{out} , ignoring the internal resistance R_s of the source E . Use voltage division.
- ii. Recalculate V_{out} taking into account the internal resistance R_s of the source. What percent error was introduced by ignoring R_s in part (i)?

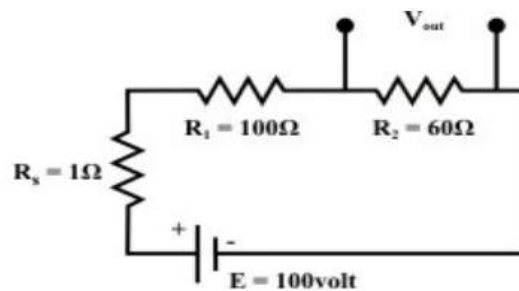


Fig. 10

(Ans: (i) $V_{out} = 37.9V$, (ii) $V_{out} = 37.27V$, Error = 1.69%)

11. Determine I_1, I_2, I_3 , and I_5 using only current divider formula in fig. 11, when $I_4 = 4A$.

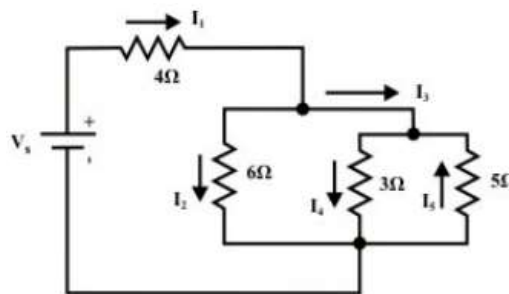


Fig. 11

($I_1 = 3.4 A$, $I_2 = 2.004 A$, $I_3 = 3.4 A$, $I_5 = 2.4 A$)

12. Consider the nonseries-parallel circuit shown in fig. 12. Determine R and the equivalent resistance R_{eq} between the terminals “a” & “b” when $V_1 = 8V$. (Hint: Applying basic two Kirchhoff's laws).

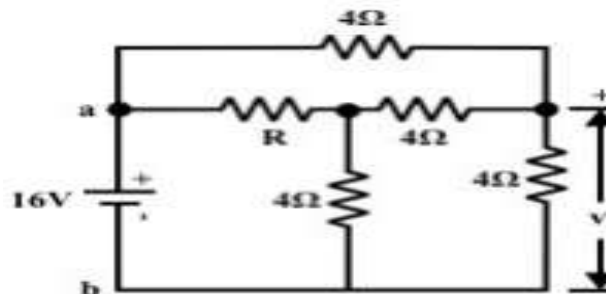


Fig. 12

(Ans: $R = 4 \Omega$, $R_{eq} = 4 \Omega$.)

13. Find equivalent resistance between the terminals ‘a’ & ‘b’ and assume all resistors values are 1Ω fig. 13.

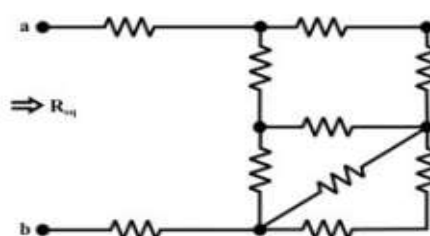


Fig. 13

14. Find the current through 'ab-branch' (I_{ab}) and voltage (V_{cg}) across the current source using Mesh-current method in Fig. 14.

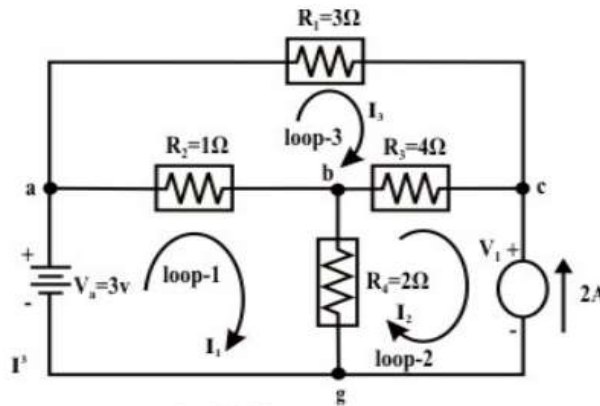


Fig. 14

(Ans: $I_{ab} = 0.39A$, $V_{cg} = 6.27V$)

15. For the circuit shown Fig. 15, find V_x using the mesh current method.

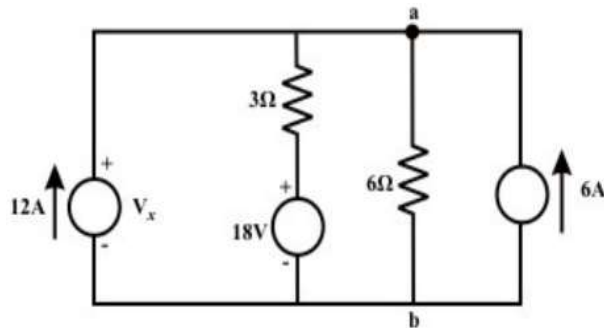


Fig. 15

(Ans: $V_x = 48V$)

16. Find the value of the current I flowing through the battery in fig.16 using 'Node voltage' method.

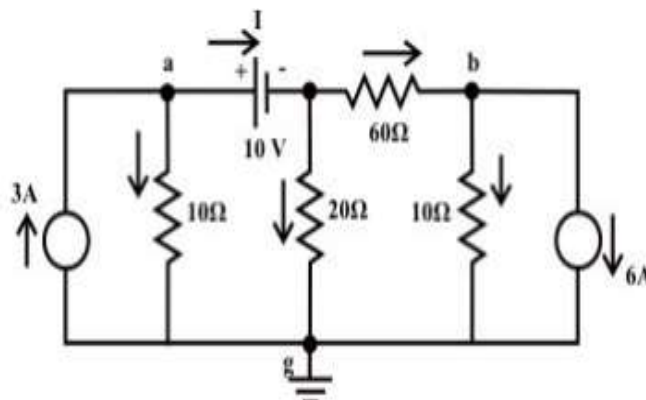


Fig. 16

(Ans: $I = 1.307A$)

....XXXXX....